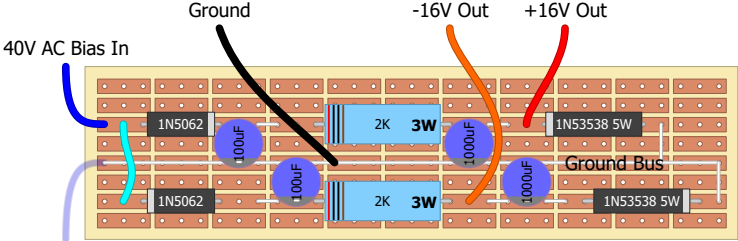


Power Solid State Devices from PT Bias Tap



40V AC transformer lead

Note diode & cap polarity

By Rob Robinette